


<https://github.com/Alsheraa313/assignment-3-310>



I worked individually

Design choices: the program counter feeds into the address input of the 16 address memory which then goes into a demultiplexer that selects the four 4 bit instruction registers. The output of the registers is then split up and taken into an instruction decoder which becomes the control signals for the register file. The register file's output become the A and B for the ALU and the extended instruction register becomes the selector pin for the ALU



Control signals: the control signals are generated by taking in the output of the extended instruction registers into the instruction decoder that takes a 2 bit input as the selector pin for a demultiplexer, and that output is split into one bit alongside a constant value zero. These two bits are then merged as an 8 bit output therefore generating a control signal for the register files


Program counter output

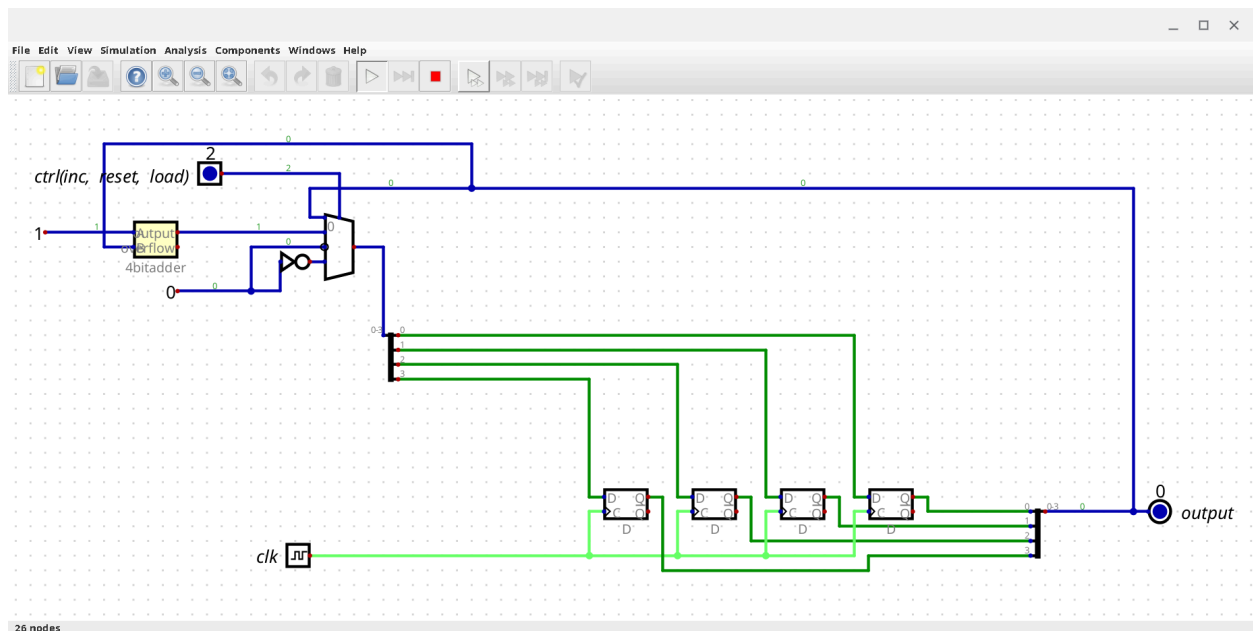

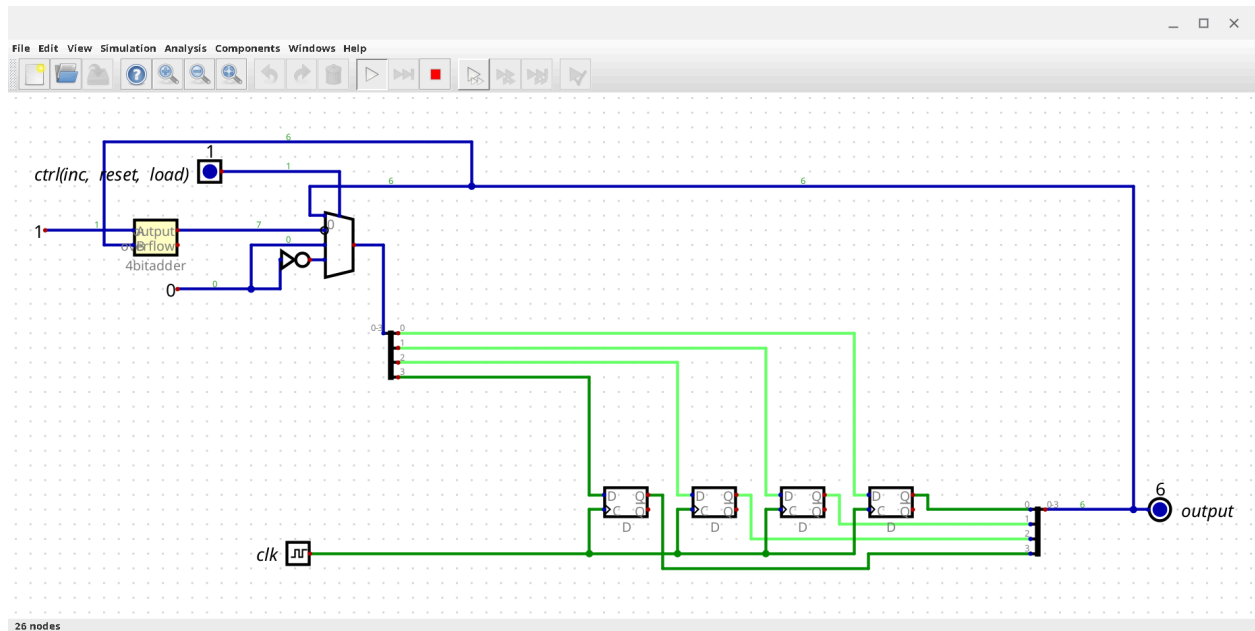
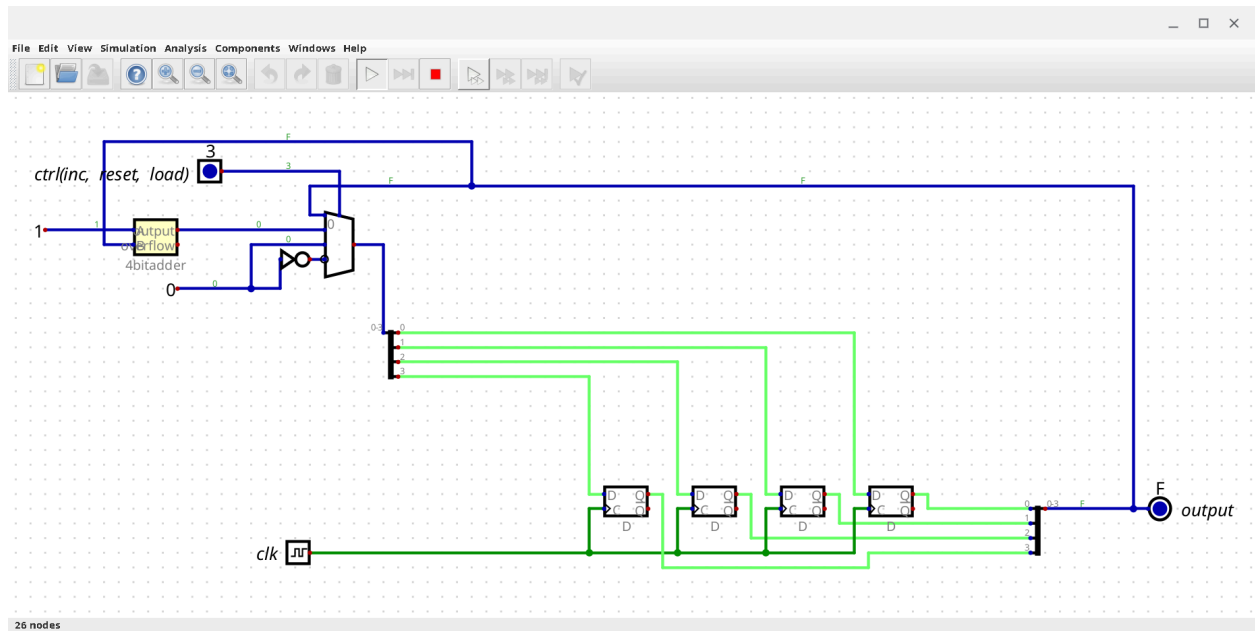




Instruction memory 16 address

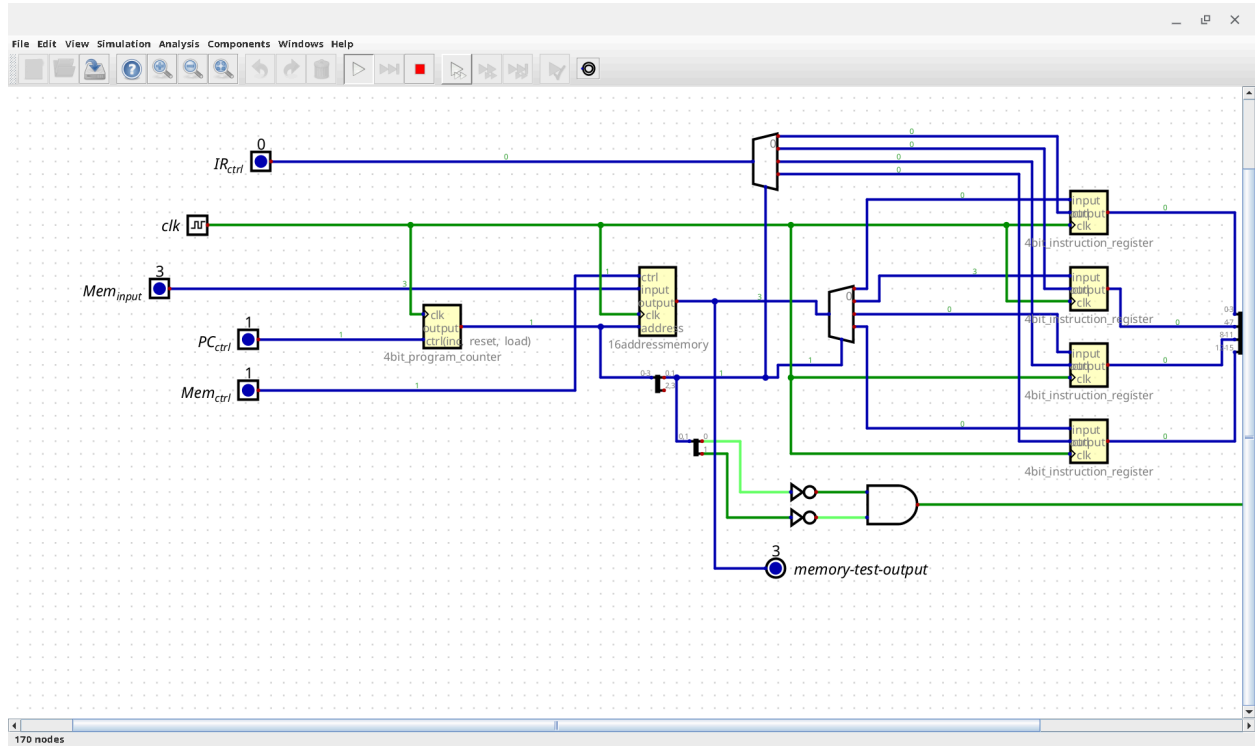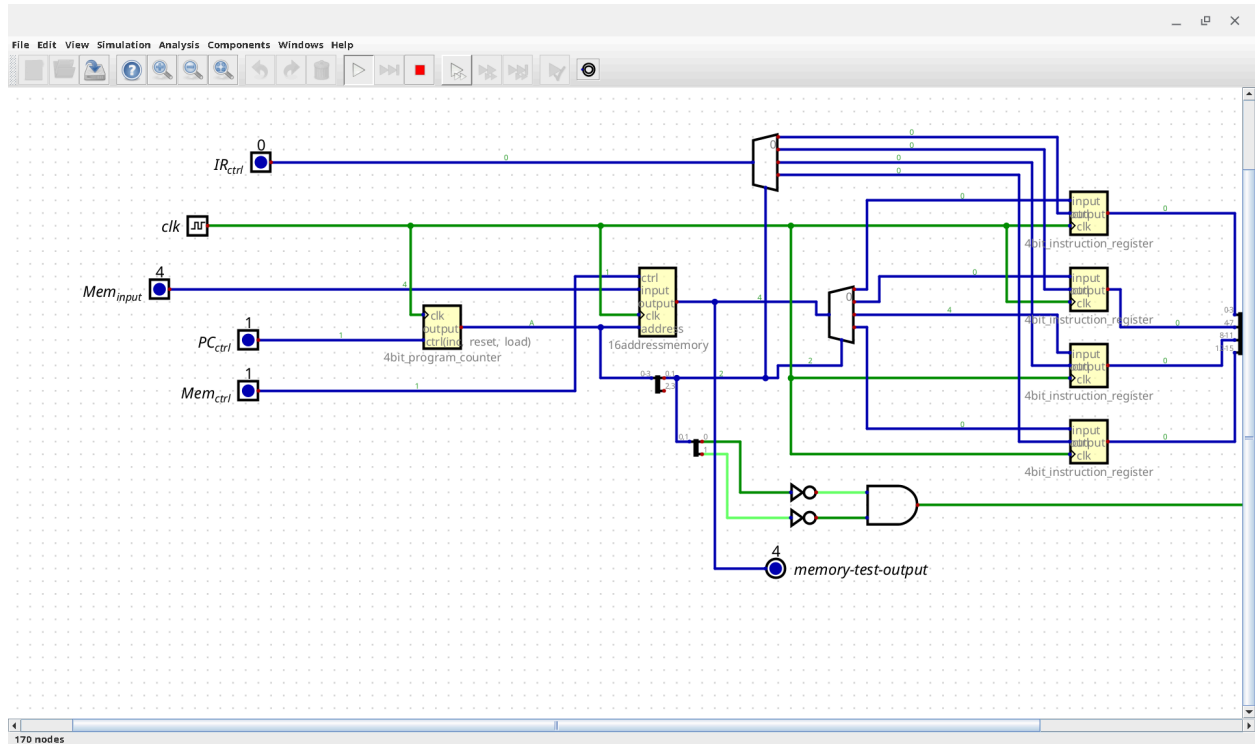


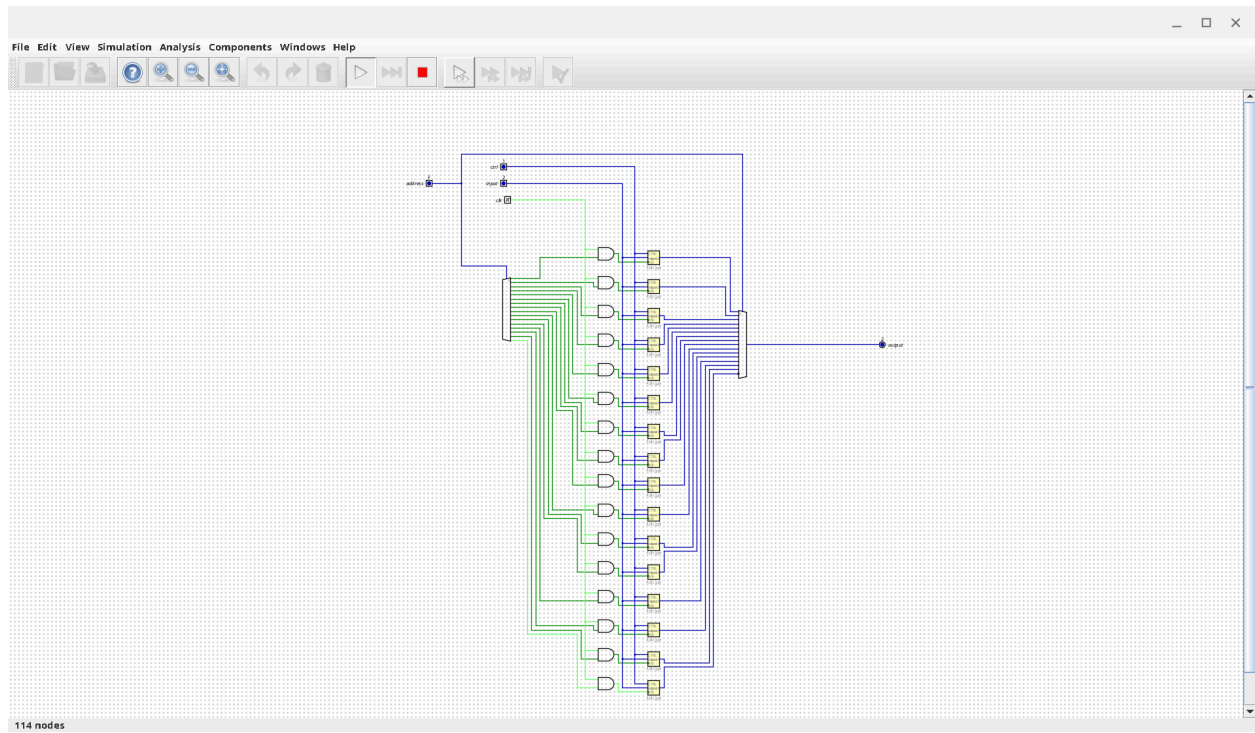


Extended IRs

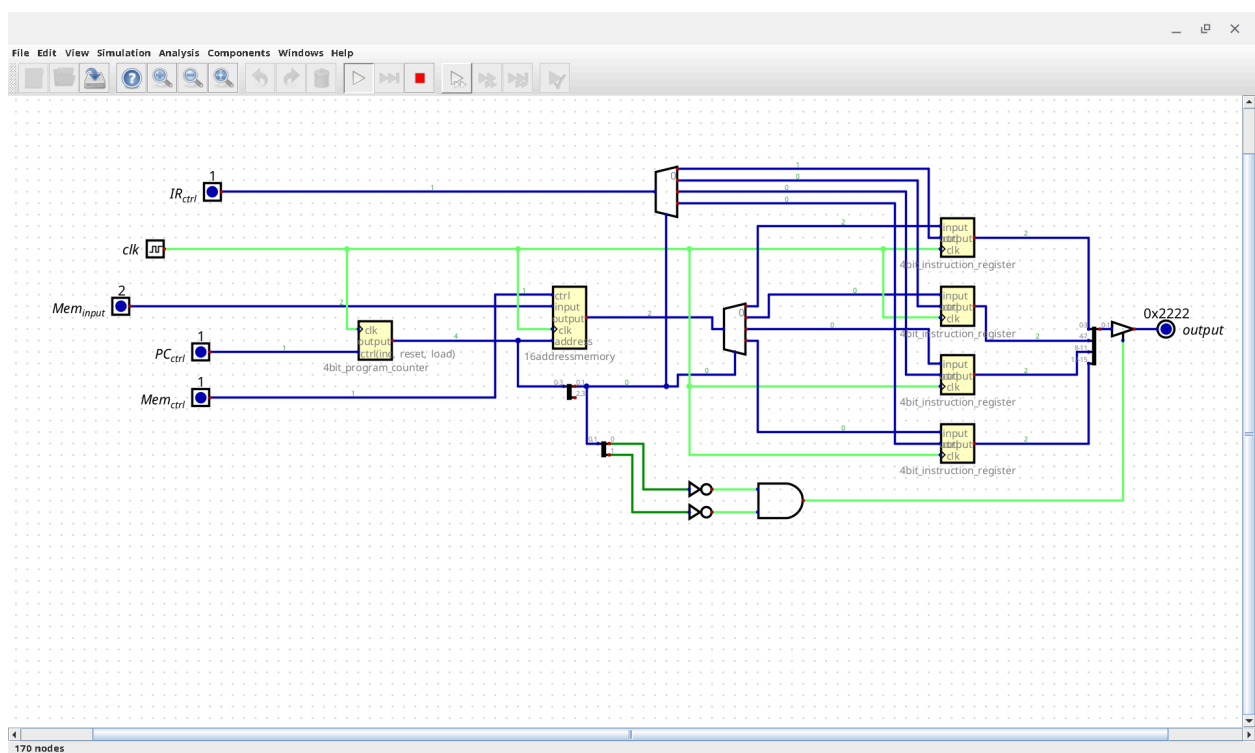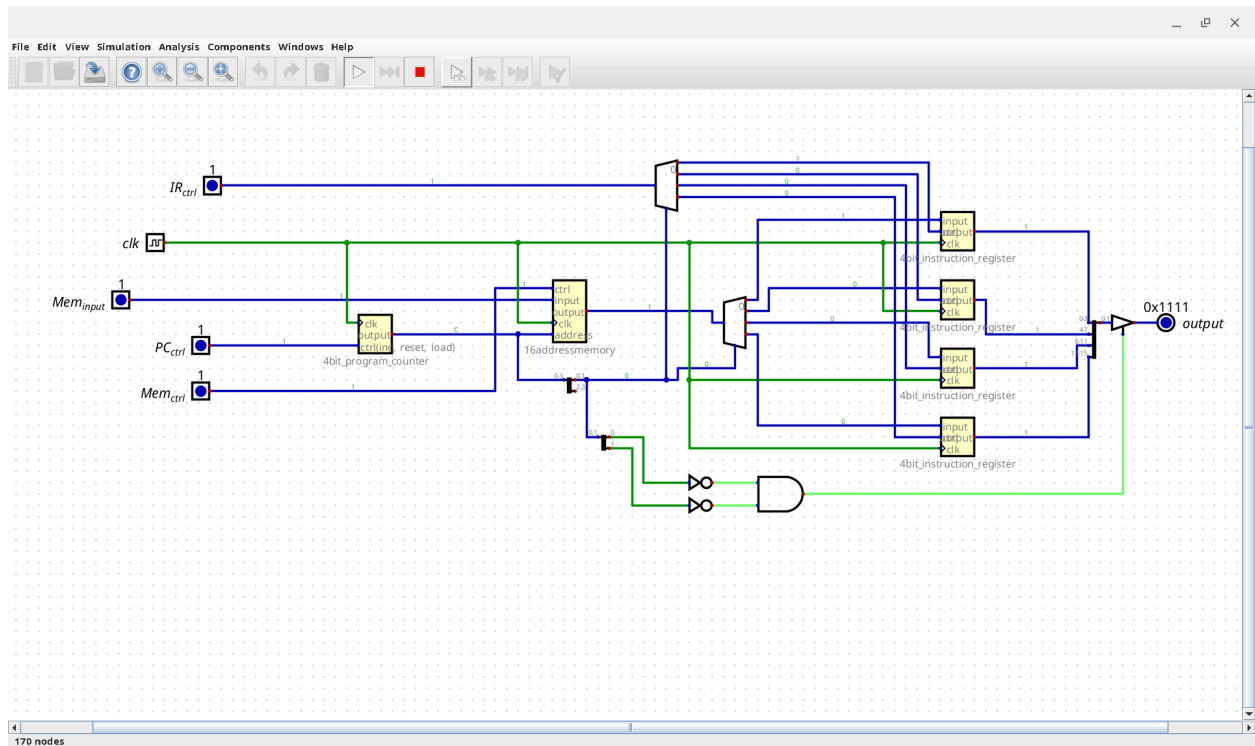

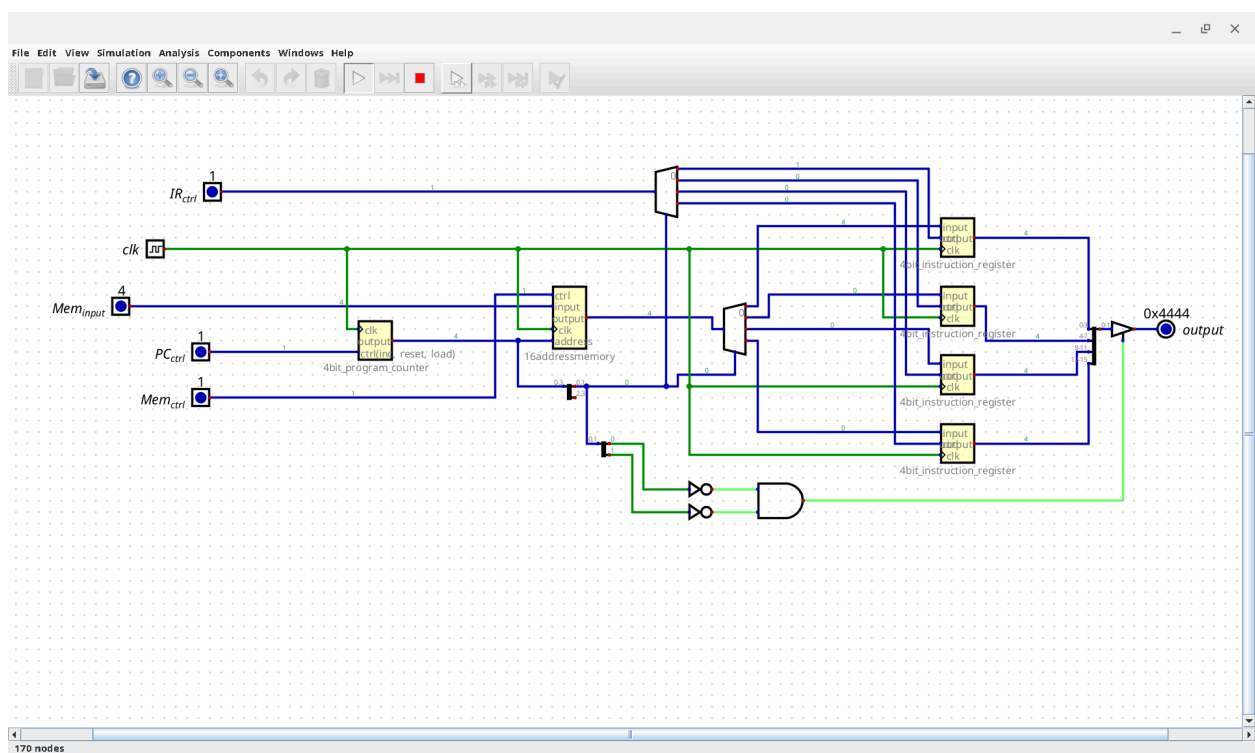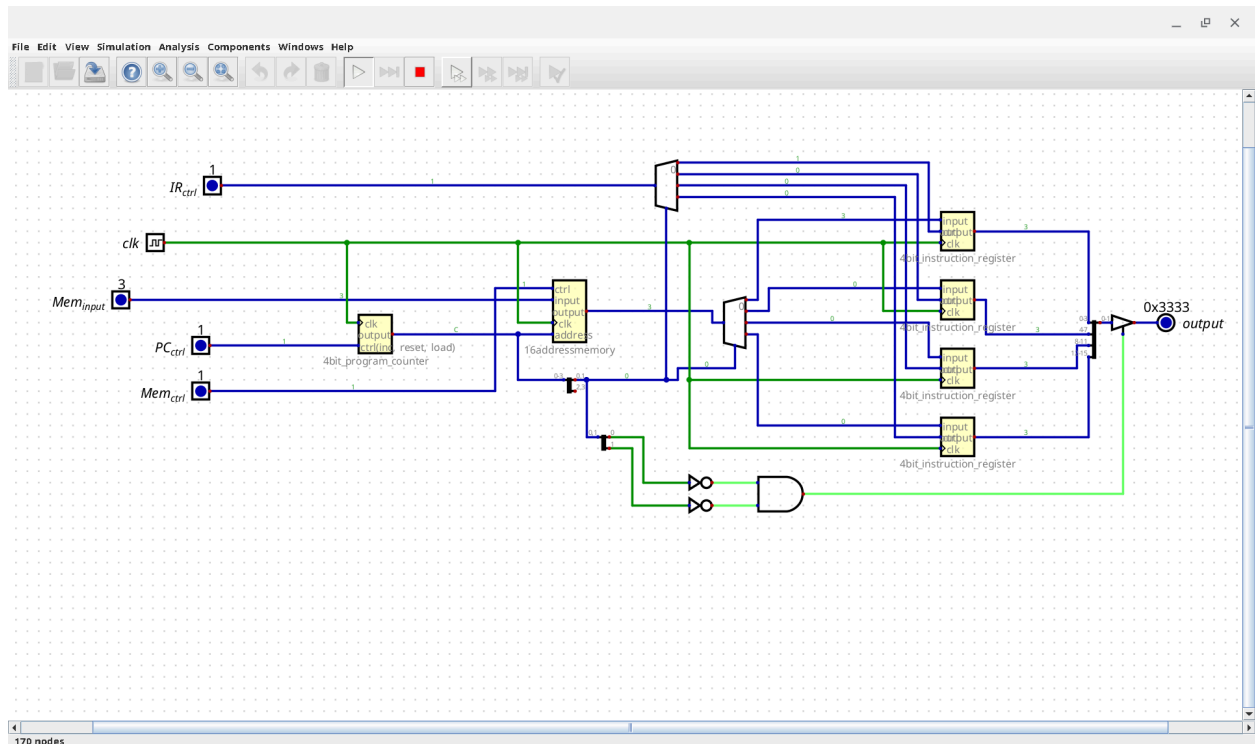


Instruction decoder / processor output

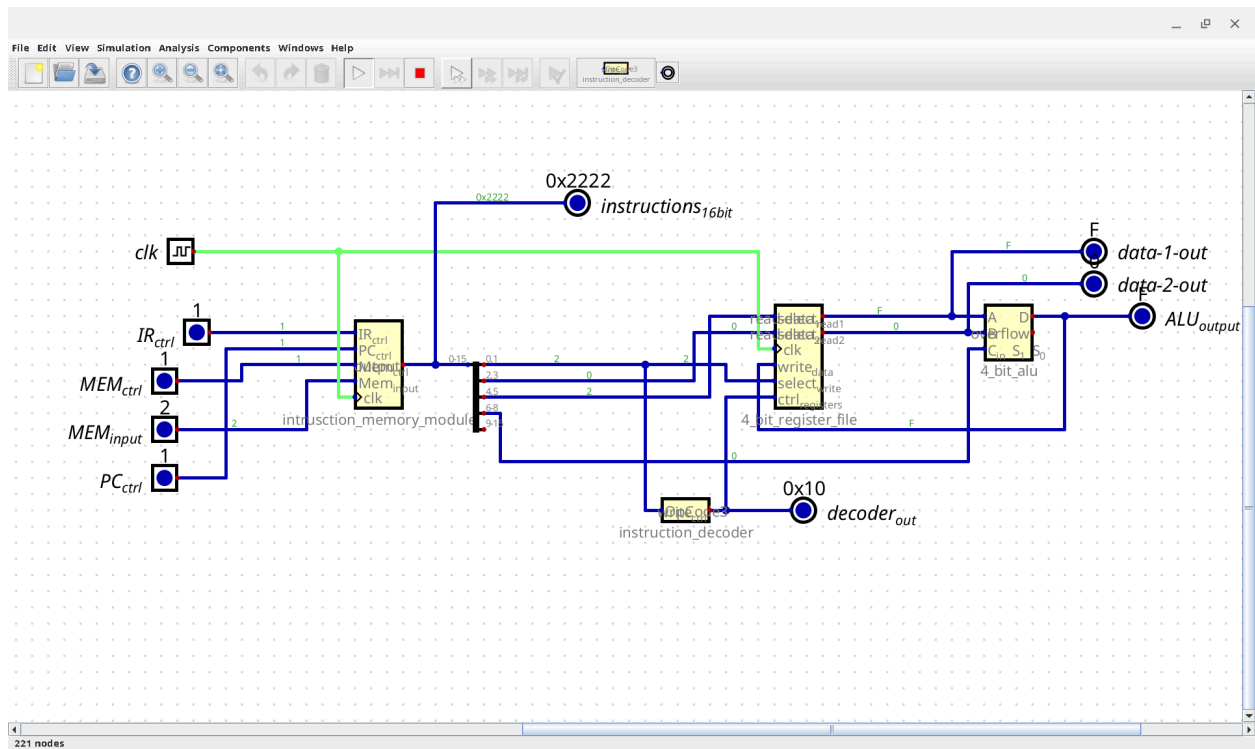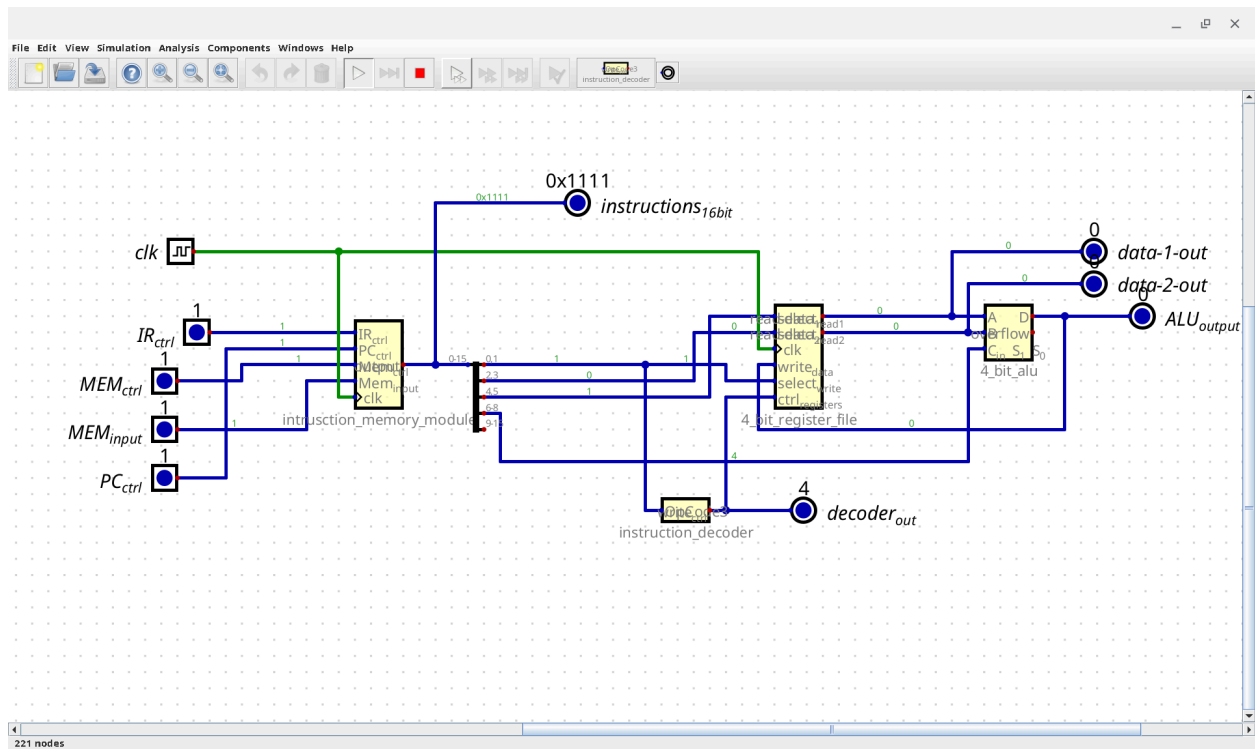


ALU operations

Add  $A + B$

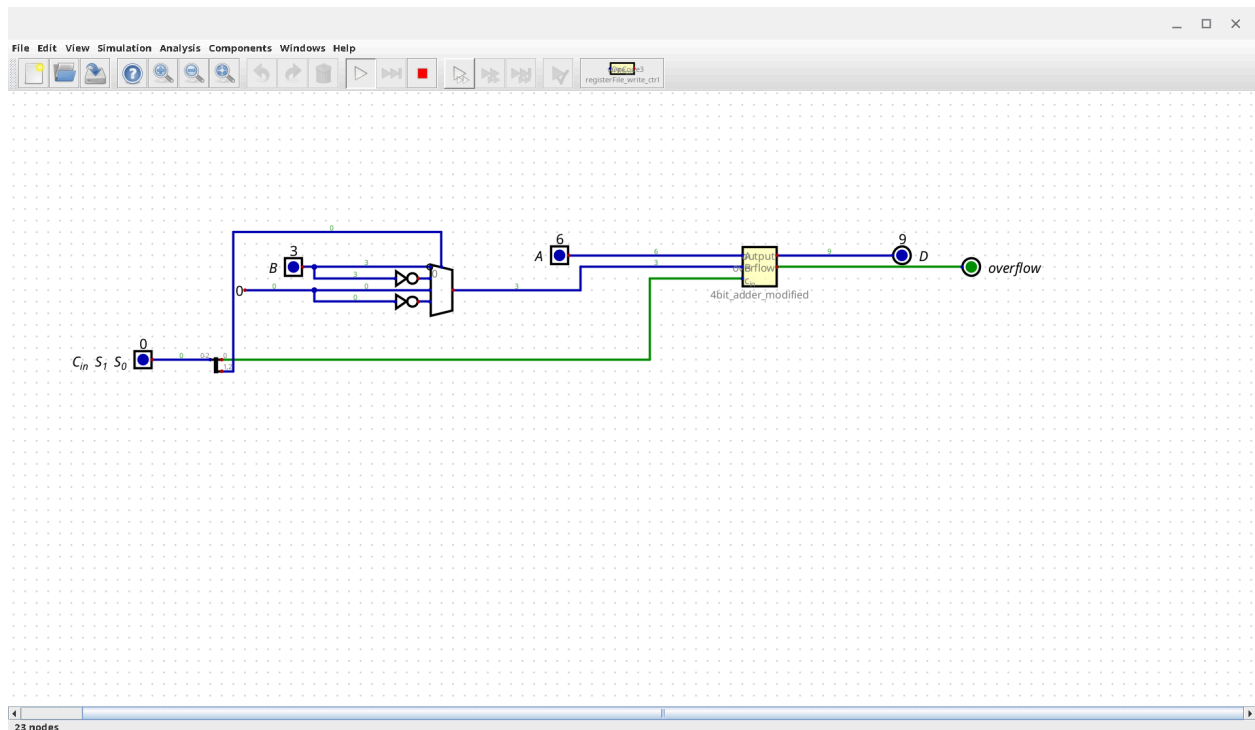


add with carry

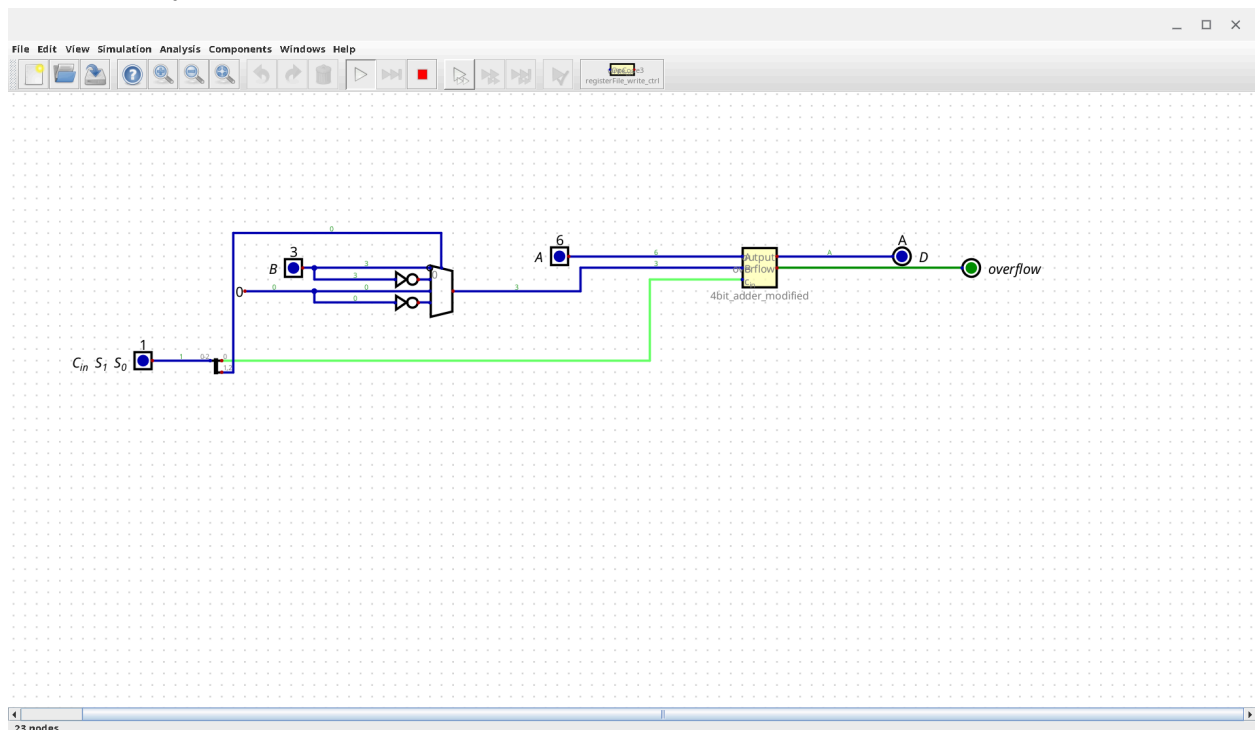





subtract A-B

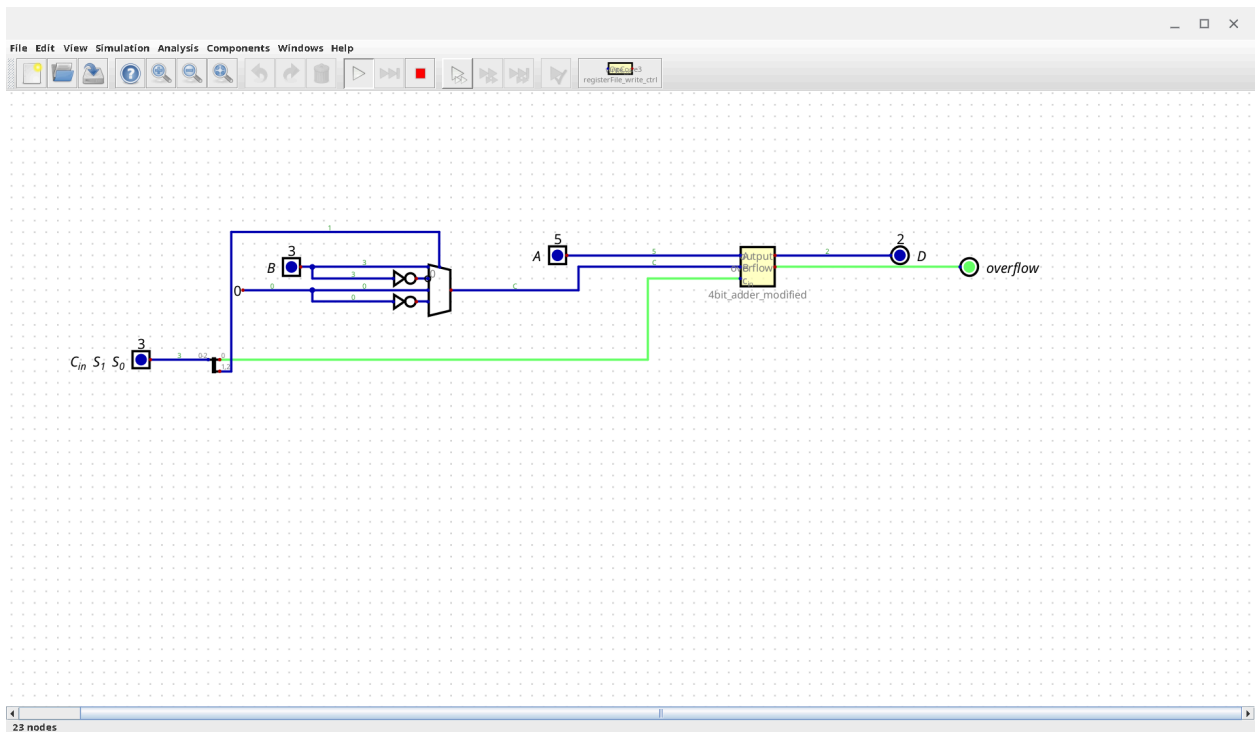

increment A

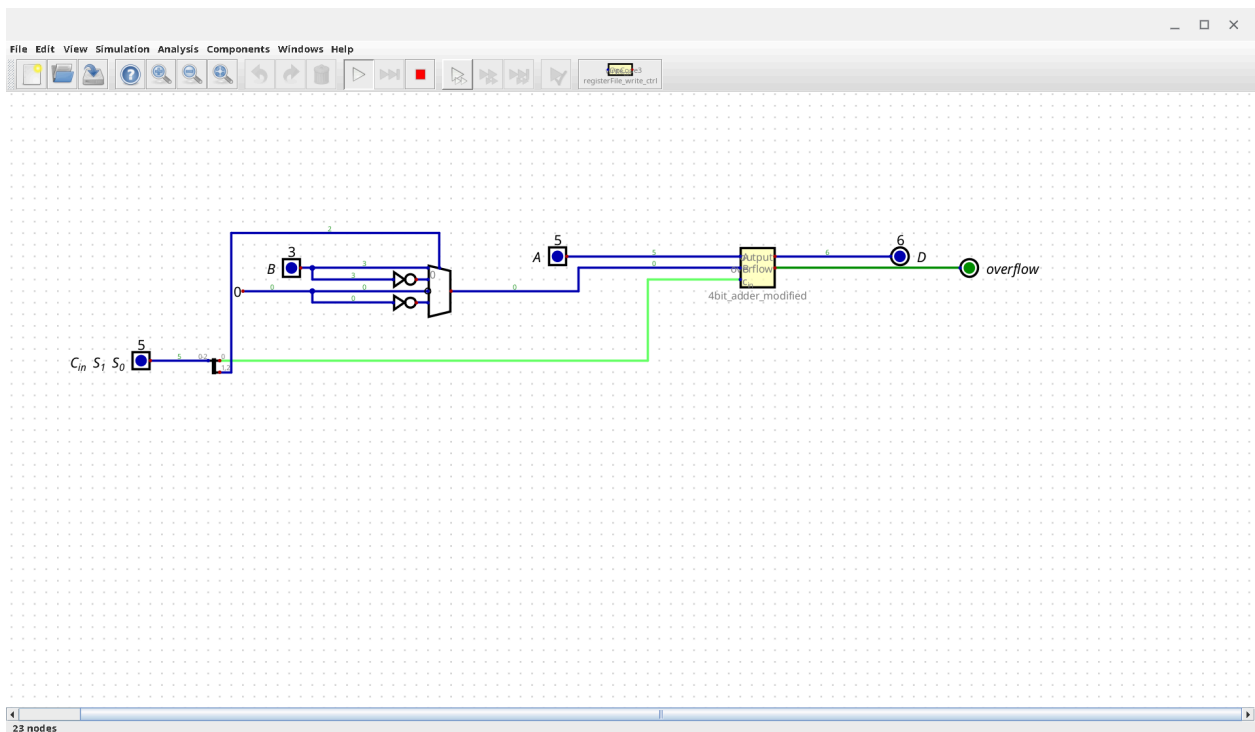

Decrement A

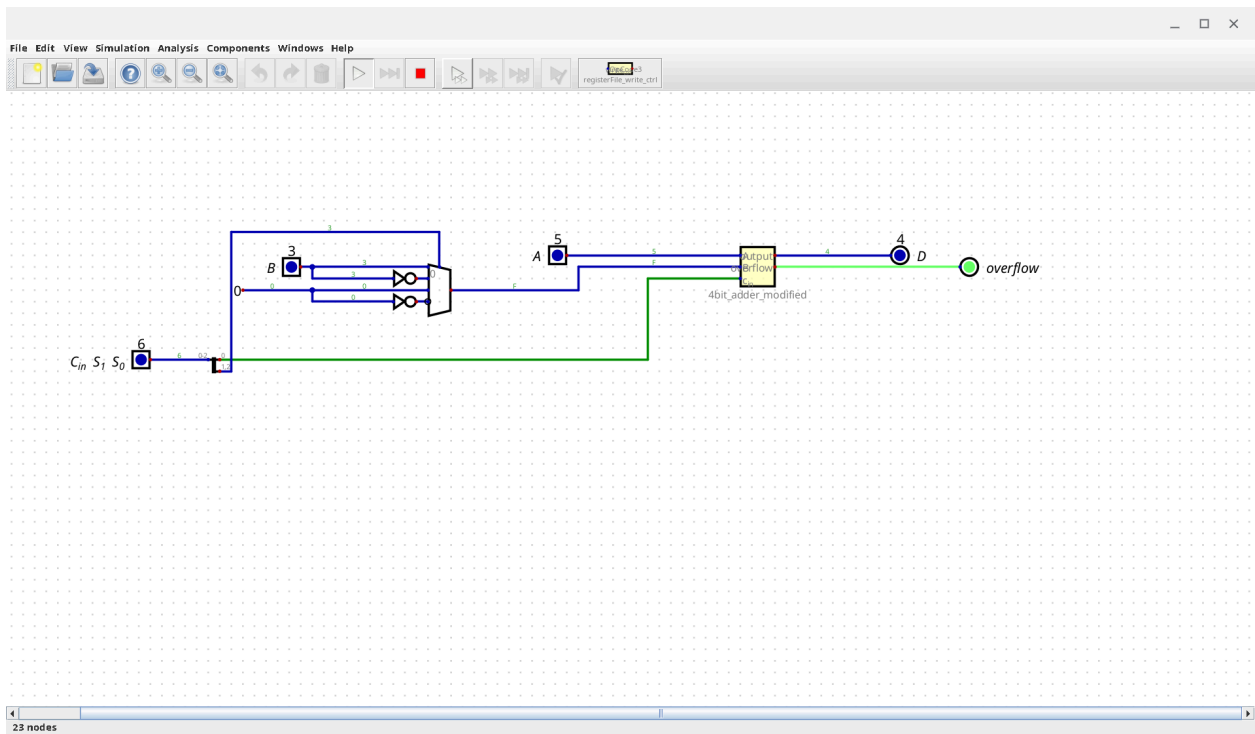

## Register files

